

## LIST OF FIGURES

Figure	Page
1.1. Cross-sectional view of one pole of a 4 pole IPM machine .....	4
1.2. Schematic diagram of an IPM generator feeding an RL load with shunt capacitors placed at the terminals of the IPM .....	4
1.3 Schematic diagram of an IPM generator feeding a 3-phase full bridge rectifier resistive load . .....	9
1.4. Schematic diagram of an IPM generator feeding a rectifier-boost-resistive load .....	9
1.5. Schematic diagram of an IPM generator feeding a rectifier-buck-resistive load ..	10
1.6. Schematic diagram of an IPM generator feeding an induction motor .....	10
2.1. Model of a brushless PM synchronous machine .....	14
2.2. Schematic diagram representing the steady state q and d axis voltage equations of a PM machine .....	24
2.3. Schematic diagram of dc test used to determine stator resistance .....	26
2.4. Measured line to neutral rms terminal generator voltage vs air gap voltage for no load condition for machine connected in high and low voltage stator connections .....	29
2.5. Measured values of q axis inductance vs peak stator current .....	32
2.6. Measured d axis inductance vs peak stator current .....	33
2.7. Measured magnetic flux vs peak stator current. ....	34
2.8. Measured q axis inductance vs peak mutual flux .....	35
3.1. IPM generator feeding an RL impedance load with capacitive compensation .....	39

Figure	Page
3.2. D Q equivalent circuit of IPM machine connected to an RLC load .....	39
3.3. Equivalent circuit of dq representation of IPM machine connected to a resistive load with shunt capacitive compensation .....	46
3.4. Equivalent circuit of IPM machine feeding a resistive load.....	49
3.5. Measured and calculated line to neutral generator voltage vs load power output for various generator frequencies .....	52
3.6. Measured and calculated generator line current vs output power for various frequencies .....	53
3.7. Measured and calculated load voltage vs load resistance.....	54
3.8. Measured and calculated output power vs load resistance for various frequencies.....	55
3.9. Measured and calculated line to line generator voltage vs stator current for various frequencies .....	56
3.10. Measured and calculated line to neutral generator voltage vs output power for PM machine with capacitor compensation .....	57
3.11. Measured and calculated generator line current vs output power for PM machine with capacitor compensation .....	58
3.12. Measured and calculated line to neutral generator voltage vs per phase load resistance for shunt capacitor scheme.....	59
3.13. Measured and calculated output power vs load resistance for capacitor compensation scheme .....	60
3.14. Measured and calculated stator current vs line to neutral generator voltage for capacitor compensation scheme .....	61
3.15. Measured and simulated line to line voltage waveforms for the generator feeding a 22 $\Omega$ resistive load. Rotor speed=1350 rpm. Measured waveform scale: voltage:50v/div, time 5ms/div. ....	63

Figure	Page
3.16. Measured and simulated generator currents waveforms for a 22 $\Omega$ load. Rotor speed=1350 rpm. Measured waveform scale: current: 1A/div, time 5ms/div...	64
3.17. Measured and simulated load currents for a 22 $\Omega$ load. Rotor speed=1350 rpm. Measured waveform scale: current: 1A/div, time 5ms/div.....	64
3.18. Measured and simulated waveforms of the line to line voltage for a 205 $\Omega$ load. Rotor speed = 1350 rpm. Measured waveform scale: voltage:50V/div, time 5ms/div .....	65
3.19. Measured and simulated waveforms of generator current for a 205 $\Omega$ load. Rotor speed=1350 rpm. Measured waveform scale: current: 200 mA/div, time 5ms/div.....	66
3.20. Measured and simulated waveforms of load current for a 205 $\Omega$ load. Rotor speed=1350 rpm. Measured waveform scale: current:100 mA/div, time 5ms/div.....	66
4.1. Schematic diagram of IPM-Rectifier feeding an impedance load.....	70
4.2. Schematic diagram of 3 phase full bridge rectifier.....	70
4.3. Measured and calculated line to neutral voltage vs output power for IPM machine. ....	79
4.4. Measured and calculated load power vs load resistance for IPM feeding a rectifier-resistive load.....	80
4.5. Measured and calculated load voltage vs generator current for IPM feeding a rectifier-resistive load.....	81
4.6. Measured and calculated load voltage vs generator output power.....	82
4.7. Measured power loss in the rectifier vs the load resistance.....	83
4.8. Resistive-Inductive model of a UI diode.....	85
4.9. Simulink model of a UI diode.....	85
4.10. Simulink representation of a UI diode.....	85

Figure	Page
4.11. Simulink model of an IU diode.....	87
4.12. Simulink representation of an IU diode.....	87
4.13. Simulink models of (a) a UI Inductor and (b) an IU capacitor.....	87
4.14. Simulink models of (a) an IU inductor and (b) a UI capacitor.....	89
4.15. Schematic diagram of full bridge rectifier with filter feeding a resistive load.....	89
4.16. Simulink model of 3-phase full bridge rectifier with filter feeding a resistive load.....	90
4.17. Simulink model of filter and resistive load.....	90
4.18. Load voltage vs time for ideal voltage source feeding rectifier.....	91
4.19. Simulated waveform of capacitor current vs time for ideal voltage source feeding a rectifier.....	92
4.20. Simulated waveform of input current into the rectifier vs time.....	93
4.21. Simulated waveform of current flowing through the inductor filter for ideal voltage source feeding a rectifier.....	94
4.22. Measured and simulated line to line voltage waveforms for the generator feeding a rectifier-resistive 22 $\Omega$ resistive load. Rotor speed=1350 rpm. Measured waveform scale: voltage:50v/div, time 5ms/div.....	96
4.23. Measured and simulated generator currents waveforms for a 22 $\Omega$ load. Rotor speed=1350 rpm. Measured waveform scale: current 2A/div, time 5ms/div.....	97
4.24. Measured and simulated rectifier input currents for a 22 $\Omega$ rectifier-resistive load. Rotor speed=1350 rpm. Measured waveform scale: current: 2A/div, time: 5ms/div.....	97
4.25. Measured and simulated capacitor currents for a 22 $\Omega$ rectifier-resistive load. Rotor speed=1350 rpm. Measured waveform scale: current:1A/div, time 5ms/div.....	98

Figure	Page
4.26. Measured and simulated waveforms of the line to line voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: voltage:50v/div, time 5ms/div. ....	99
4.27. Measured and simulated waveforms of the generator line current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current:500mA/div, time 5ms/div. ....	99
4.28. Measured and simulated waveforms of the input rectifier current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current:500 mA/div, time 5ms/div. ....	100
4.28. Measured and simulated waveforms of the a.c. capacitor current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current: 500 mA/div, time 5ms/div. ....	101
4.30. Measured and simulated waveforms of the line to line generator voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: voltage: 50 V/div, time 5ms/div. ....	102
4.31. Measured and simulated waveforms of the generator current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: current: 1A/div, time 5ms/div. ....	102
4.32. Fast Fourier transform of measured and simulated waveforms of the generator line to line voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. ....	103
4.33. Fast Fourier transform of measured and simulated waveforms of the generator line current for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. ....	104
4.34. Measured and simulated waveforms of the load voltage for a 132 ohm rectifier-resistive load. Rotor speed = 1350 rpm. Measured waveform scale: voltage: 5V/div, time 200ms/div. ....	105
5.1. Basic dc-dc converter and associated voltage output .....	107
5.2. Dc-dc (buck) converter with low pass filter .....	108

Figure	Page
5.3. Control signal and saw tooth voltage waveforms and switching signal sent to turn switch on and off.....	109
5.4. Schematic diagram of comparators and op-amp used to control the signal of a converter .....	109
5.5. Inductor current and switching functions for the buck converter.....	110
5.6. Schematic diagram of an IPM generator feeding a rectifier-buck-resistive load .....	111
5.7. Buck converter in mode 1 operation.....	111
5.8. Buck converter in modes 2 and 3.....	111
5.9. Effective resistance vs duty cycle for buck converter .....	124
5.10. Source (input) current vs duty cycle for buck converter .....	125
5.11. Input power vs duty cycle for buck converter .....	126
5.12. Load voltage vs duty cycle for buck converter.....	127
5.13. Measured and calculated generator line to neutral voltage vs generator output power for the IPM feeding a rectifier-buck resistive load.....	129
5.14 Measured and calculated generator line to neutral voltage vs duty ratio for the IPM feeding a rectifier-buck resistive load.....	130
5.15 Measured and calculated rectifier voltage vs duty ratio for the IPM feeding a rectifier-buck-resistive load .....	131
5.16. Measured and calculated rectifier voltage vs duty ratio for the IPM feeding a rectifier-buck-resistive load.....	132
5.17. Measured and calculated generator current vs duty ratio for the IPM feeding a rectifier-buck-resistive load .....	133
5.18. Measured and calculated load voltage vs duty ratio for the IPM feeding a rectifier-buck-resistive load .....	134

Figure	Page
5.19. Plot of converter efficiency vs duty ratio for the IPM feeding a rectifier-buck-resistive load topology .....	135
5.20 Measured power loss vs duty ratio for the IPM feeding a rectifier-buck resistive load .....	136
5.21. Simulink model of a UI transistor.....	138
5.22. Simulink model of an IU transistor.....	138
5.23. Simulink symbolic representations of (a) a UI transistor and (b) an IU transistor .....	139
5.24. Generation of switching scheme for transistor. (a) a dc signal superimposed upon a triangle wave, (b) signal sent to transistor .....	139
5.25. Measured and simulated line to line voltage waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage:50v/div, time 10ms/div. ....	141
5.26. Measured and simulated generator current waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 1A/div, time 5ms/div. ....	142
5.27. Measured and simulated buck inductor current waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .1A/div, time .2ms/div .....	142
5.28. Measured and simulated buck transistor current waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 1A/div, time .2ms/div.....	143
5.29. Measured and simulated generator line to line voltage waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage: 50v/div, time 2ms/div. ....	144
5.30. Measured and simulated generator line current waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .5A/div, time 2ms/div .....	145

Figure	Page
5.31. Measured and simulated inductor current waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 5A/div, time .2ms/div.....	146
5.32. Measured and simulated transistor current waveforms for the generator feeding a rectifier-buck-resistive 10Ω resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 2A/div, time .2ms/div.....	146
6.1. Inductor current and switching functions for the boost converter.....	148
6.2. Schematic diagram of an IPM generator feeding a rectifier-boost-resistive load .....	149
6.3. Schematic diagram of a boost converter in mode 1 operation.....	149
6.4. Schematic diagram of a boost converter in modes 2 and 3.....	149
6.5. Effective resistance vs duty cycle for a boost converter.....	160
6.6. Source (input) current vs duty cycle for a boost converter .....	161
6.7. Input power vs duty cycle for a boost converter.....	162
6.8. Load voltage vs duty cycle for a boost converter .....	163
6.9. Measured and calculated generator line to neutral voltage vs generator output power for the IPM feeding a rectifier-boost-resistive load .....	165
6.10. Measured and calculated generator line to neutral voltage vs duty ratio for IPM generator feeding rectifier-boost-resistive load .....	166
6.11. Measured and calculated rectifier voltage vs duty ratio for IPM generator feeding a rectifier-boost resistive load.....	167
6.12. Measured and calculated generator output power vs duty ratio for IPM generator feeding rectifier-boost-resistive load .....	168
6.13. Measured and calculated generator current vs duty ratio for IPM generator feeding rectifier-boost-resistive load .....	169



Figure	Page
6.14. Measured and calculated load voltage vs duty ratio for IPM generator feeding a rectifier-boost-resistive load .....	170
6.15. Measured power loss of rectifier-boost system vs the duty ratio .....	171
6.16(a). Measured converter efficiency vs duty ratio for IPM generator feeding rectifier-boost-resistive load .....	172
6.16(b). Measured and calculated rectifier-boost effective resistance vs duty ratio .....	174
6.17. Measured and simulated line to line voltage waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage:20v/div, time 10ms/div. ....	176
6.18. Measured and simulated generator current waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 2A/div, time 10ms/div.....	176
6.19. Measured and simulated boost inductor current waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .2A/div, time .2ms/div .....	177
6.20. Measured and simulated rectifier output current waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale: current: .2A/div, time 2ms/div .....	177
6.21. Measured and simulated generator line to line voltage waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed equals 900 rpm .Measured waveform scale: voltage: 20v/div, time 10ms/div....	178
6.22. Measured and simulated generator line current waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale: current: 2A/div, time 10 ms/div.....	179
6.23. Measured and simulated inductor current waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale:current: 5A/div, time .2ms/div.....	180

Figure	Page
6.24. Measured and simulated rectifier output current waveforms for the generator feeding a rectifier-boost-resistive $77\Omega$ resistive load. Rotor speed=900 rpm. Measured waveform scale: voltage: .2A/div, time 2ms/div .....	181
7.1. Schematic diagram of IPM machine feeding an induction machine .....	184
7.2. DQ representation of induction machine with capacitive compensation .....	184
7.3. Schematic diagram of (a) per phase equivalent circuit, (b) short circuit equivalent circuit, (c ) simplified short circuit equivalent circuit, (d) no load equivalent circuit for induction machine .....	191
7.4. Plot of mutual inductance vs mutual flux linkage for induction motor .....	195
7.5. Plot of core loss vs mutual flux linkage for induction motor .....	195
7.6. Plot of rotor resistance vs mutual flux linkage for induction motor .....	196
7.7. Plot of leakage inductance vs mutual flux linkage for induction motor .....	196
7.8(a). Measured and calculated load torque of induction motor for three different frequencies .....	197
7.8(b). Measured and calculated peak generator output voltage vs motor speed for three operating frequencies .....	198
7.9(a). Measured and calculated peak motor input current vs motor speed .....	199
7.9(b). Measured and calculated motor input power factor vs motor speed For various operating frequencies.....	200
7.10(a). Measured and calculated motor input power vs motor speed for three operating frequencies.....	201
7.10(b). Measured and calculated peak phase generator voltage vs motor input power .....	202
7.11. Measured and calculated peak generator voltage vs peak motor input current.....	203

Figure	Page
7.12. Simulated waveforms of (a) generator current, and (b) generator voltage, (c) motor input (stator) current, (d) motor rotor current for IPM-IM topology operating under fan type load .....	207
7.13. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under fan type load .....	208
7.14. Simulated waveforms of (a) generator current, (b) generator voltage, (c) motor input current, and (d) motor rotor current for IPM-IM topology operating under type b load.....	212
7.15. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under type b load.....	213
7.16. Simulated waveforms of (a) generator current, (b) generator voltage, (c) motor input current, and (d) motor rotor current for IPM-IM topology operating under type b load.....	214
7.17. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under type b load .....	215
7.18. Simulated waveforms of (a) generator current, and (b) generator voltage, (c) motor input ( stator ) current, (d) motor rotor current for IPM-IM topology operating under type c load.....	218
7.19. Simulated waveforms of (a) motor speed, (b) load torque, (c) motor electromagnetic torque, (d) electromagnetic and load torque vs motor speed for IPM-IM topology operating under type c load .....	219